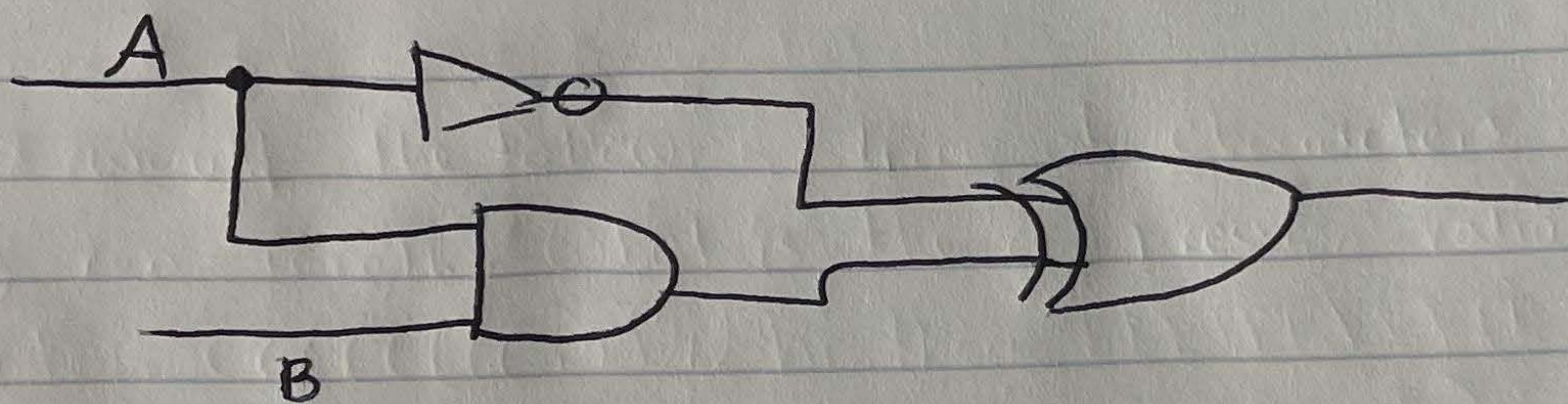
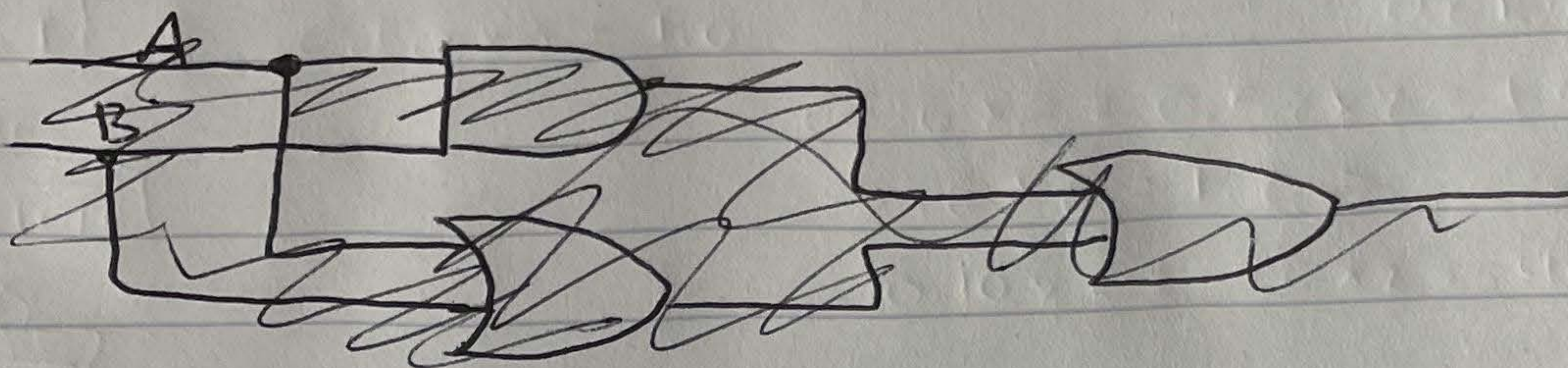


61.) Show the behavior of the following circuit with a truth table.



A	B	X
0	0	0
0	1	1
1	0	1
1	1	0