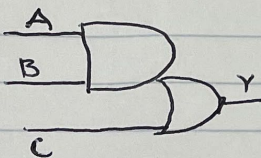


3.) A three-input AND-OR (Ao) gate shown in Figure 2 produces a TRUE output if both A and B are TRUE, or if C is TRUE. Complete a truth table for the gate.

Figure 2:



A	B	C	output
0	0	0	0
0	0	1	1
0	1	0	0
1	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1
1	1	1	1